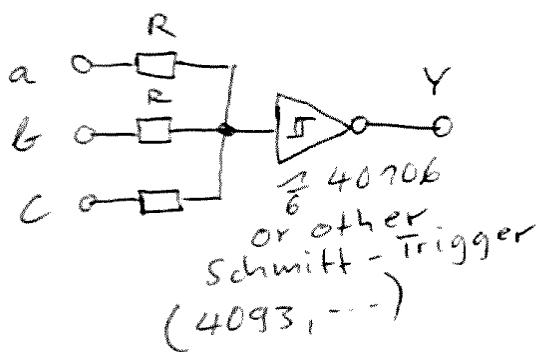


SINGLE CHIP (40106) RINGMODULATOR SOUND MODULE

(inverting, of course)


This is a ⁺ NEURON
sometimes called
"majority gate"



c	b	a	Y
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

if $c = \emptyset$
a, b behave
like a $\overline{\text{NAND}}$

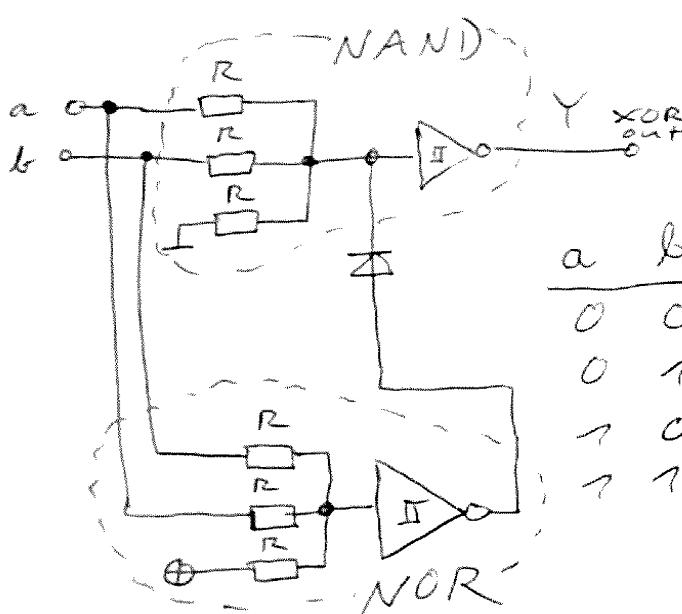if $c = 1$
a, b behave
like a $\overline{\text{NOR}}$



if we force the
 $a, b = 0, 0$ condition to
 $a, b = 1, 1$ with the help of a NOR
and a diode - we can convert the
NAND to an XOR

a	b	XOR	
		NAND	XOR
0	0	1	0
0	1	1	1
1	0	1	1
1	1	0	0

Now we use $\frac{1}{3}$ 40106 or $\frac{1}{2}$ 4093 to create an XOR.

Let's use the rect to make some oscillators and create a 7-chip

Cumettic RING MODULATOR sound module:

