
4070 XOR gate at 5v

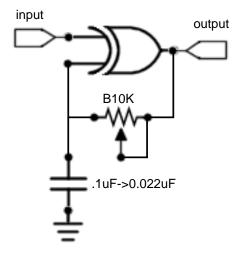(work in progress) super simple filter, also works with 4077 XNOR and 4011 NANE



free use for everyone, tjookum 2010